

**Q1.** The Boolean equation for a particular logic circuit with inputs A and B and output Q is:

$$Q = (A \cdot B) + (\bar{A} \cdot \bar{B})$$

- (a) The table below shows intermediate logic signals for the circuit, and the overall output, Q, for all combinations of the inputs A and B.

Complete the missing two entries in the truth table.

A	B	$\bar{A}$	$\bar{B}$	A . B	$\bar{A} \cdot \bar{B}$	Q
0	0	1	1	0	1	
0	1	1	0	0	0	0
1	0	0	1	0		0
1	1	0	0	1	0	1

(1)

- (b) Complete the diagram in the figure below to show the logic circuit that has the same function as the Boolean equation given above. Your circuit should contain only **two** AND gates, **two** NOT gates, and **one** OR gate.

A ○ ———

B ○ ———

—————○ Q

(3)

(Total 4 marks)

**Q2.** A fridge is fitted with a temperature-sensing unit to indicate whether the temperature inside the fridge is too high, too low, or at a safe temperature.

The system consists of a temperature sensor that produces a 2-bit binary output, a logic circuit and a low current, common cathode 7-segment display.

**Figure 1** shows a block diagram of the system.

**Figure 1**

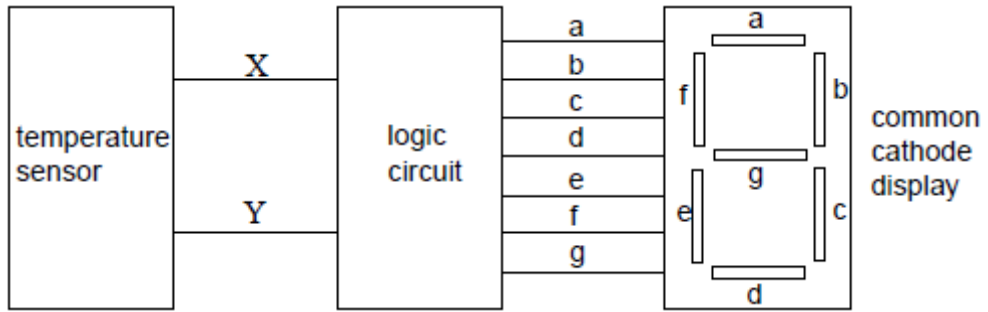


Table 1 shows the operation of the system.

Table 1

Fridge temperature	Temperature sensor output		7-segment display output
	X	Y	
< 3 °C	0	0	L
3 °C to 4 °C	0	1	S
4 °C to 5 °C	1	0	S
> 5 °C	1	1	H

**Key**

L = low

S = safe

H = high

- (a) Complete **Table 2** to show the logic signals required on lines a to g to display the specified characters.

Table 2

X	Y	a	b	c	d	e	f	g	Display
0	0								L
0	1								S
1	0								S
1	1								H


(b) Circle the single logic gate which would generate the required signal for segment a.

AND      EXOR      OR      NAND      NOR      NOT

(1)

(c) The LEDs in the 7-segment display must be protected by current limiting resistors. **Figure 2** shows two methods, **A** and **B**, of connecting current limiting resistors.

**Figure 2**

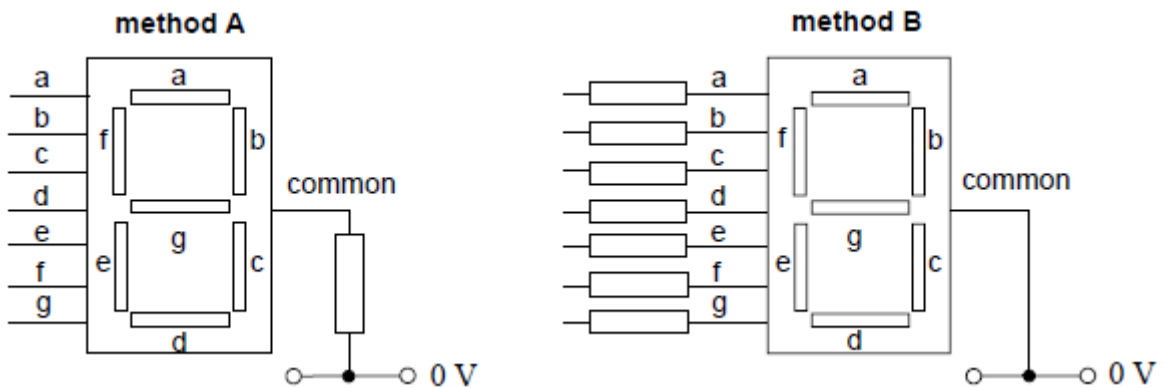

(i) State **one** disadvantage of **method A**.

.....  
 .....

(1)

(ii) Calculate the value of the current limiting resistors required in **method B** to limit the current in each segment to 20 mA. Assume the voltage from the logic circuit is 5 V and the forward voltage drop across each LED in the 7-segment display is 2.2 V.

.....  
 .....

(2)

(iii) Circle the appropriate value for these resistors from the following list of E24 resistors.

110 Ω

150 Ω


270 Ω

1.1 kΩ

1.5 kΩ

(1)  
(Total 8 marks)

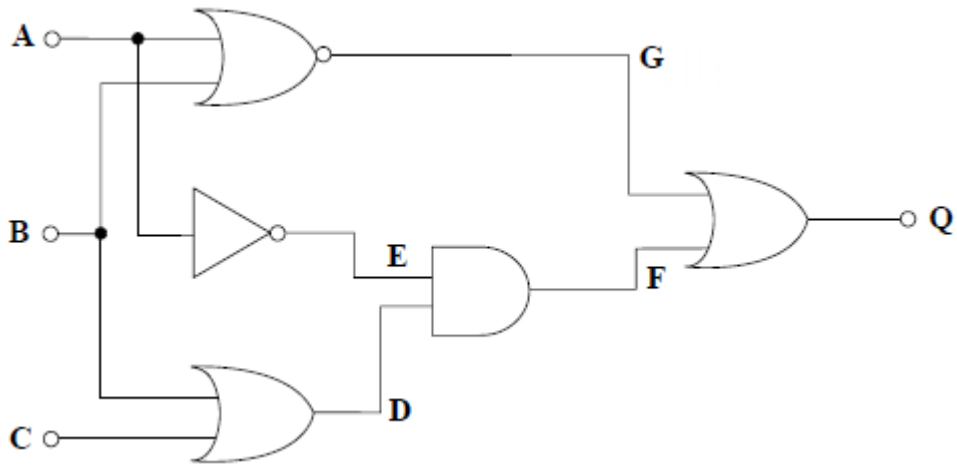**Q3.** The diagram shows a logic circuit with three inputs **A**, **B** and **C**.



- (a) Write the Boolean expressions for the signals at the intermediate points **D**, **E**, and **G** in terms of the inputs **A**, **B** and **C** only.

**D** .....

**E** .....

**G** .....

(3)

- (b) Complete the truth table below for the logic signals at the intermediate points **D**, **E** and **G**.


Inputs			Intermediate points		
<b>C</b>	<b>B</b>	<b>A</b>	<b>D</b>	<b>E</b>	<b>G</b>

0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

(5)  
(Total 8 marks)

**Q4.**Figure 1 shows a simplified diagram of a road safety system for traffic travelling towards a road tunnel. The tunnel is too narrow for two-way traffic and too low for lorries.

**Figure 1**

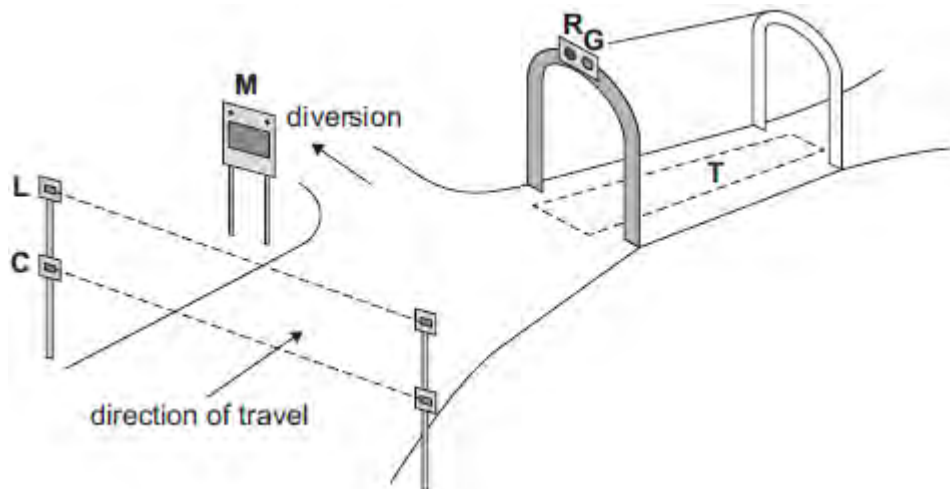

**C** and **L** are laser beam sensors placed at different heights on the road just before the tunnel. When a beam is broken, the sensor produces a logic 1.

Cars will break the beam at sensor **C only**. Lorries will break the beams at both sensor **L** and sensor **C**.

**M** is an electronic message display that tells lorries to take a diversion. The message display lights up when it receives a logic 1.

**T** is a sensor buried in the road inside the tunnel. It produces a logic 1 when an oncoming car is in the tunnel.

The red stop light **R** comes on when a lorry is detected or when there is an oncoming car in the tunnel. **R** will light up when it receives a logic 1.

The green go light **G** comes on when a car is detected and there are no oncoming cars in the tunnel. **G** will light up when it receives a logic 1.

- (a) Complete the truth table.  
Some of the data has already been entered for you.

Input			Output		
Sensor <b>T</b>	Sensor <b>C</b>	Sensor <b>L</b>	Message display <b>M</b>	Red stop light <b>R</b>	Green go light <b>G</b>
0	0	0	0	0	1
0	0	1	0	0	1
0	1	0		0	
0	1	1		1	
1	0	0		1	
1	0	1	0	1	0
1	1	0		1	
1	1	1		1	

(4)

- (b) Write the simplest Boolean expression for the red stop light **R** in terms of **T**, **C** and **L**.

.....

(2)

- (c) The expression for the green go light **G** could be written as  $G = \bar{T} \cdot (\bar{C} + \bar{L})$

Draw on **Figure 2** the logic diagram for this expression using only NOT, AND and OR gates.

Figure 2

T ○ —


C ○ —

L ○ —

G

(3)  
(Total 9 marks)

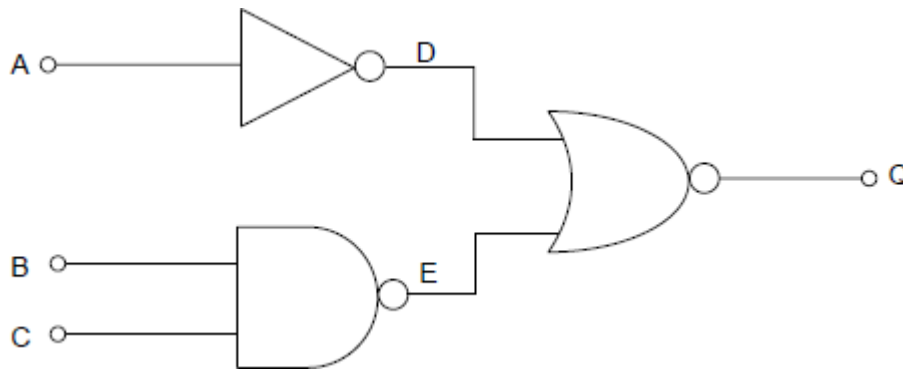Q5. As part of his project, a student constructs the following logic circuit.



(a) Write down the Boolean expressions for:

D = ..... (1)

E = ..... (2)

(b) Write down the Boolean expression for Q in terms of D and E.

Q = ..... (2)

(c) Complete the truth table below for the logic circuit above.

A	B	C	D	E	Q
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

(4)


- (d) His supervisor suggests that the logic circuit can be simplified. What single logic gate would have the same function as the whole circuit above?

.....

(1)

(Total 10 marks)

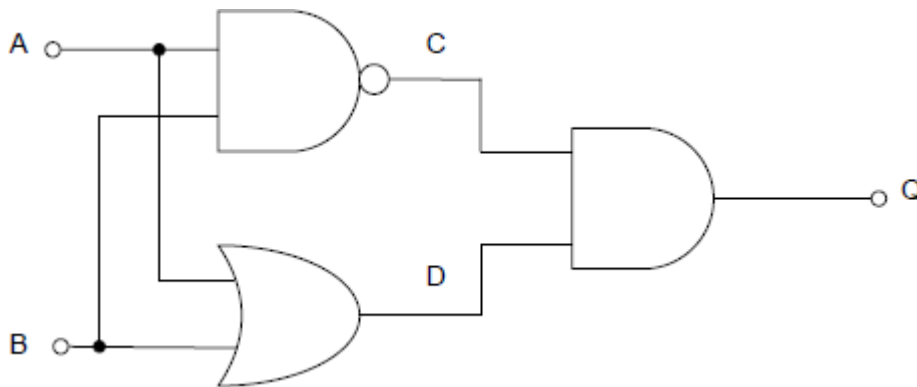**Q6.** A student constructs a circuit from the following logic diagram.



- (a) Complete the truth table below for this logic diagram.

A	B	C	D	Q
0	0			



0	1			
1	0			
1	1			

(3)

- (b) Write down Boolean expressions for the logic signals at C, D and Q in terms of the inputs A and B.

C = .....

(1)

D = .....

(1)

Q = .....

(2)

- (c) What single logic gate could perform the function of the whole circuit above?

.....

(1)

**(Total 8 marks)**