

M1.D

[1]

M2.D

[1]

M3.A

[1]

M4.C

[1]

M5.B

[1]

M6.D

[1]

M7.A

[1]

M8.D

[1]

M9.B

[1]

M10.D

[1]

M11.C

[1]

M12. B

[1]

M13. (i) C

B1

1

(ii) B

B1

1

[2]

M14. C

[1]

M15. (a) the (total) energy transferred/work done when one unit/coulomb of charge

B1

is moved around a circuit/provided by the supply

B1

2

(b) work is done inside the battery/there is resistance inside the battery

B1

so less energy is available for the external circuit/some voltage is lost between the terminal/mention of lost volts

B1

2

(c) (i) 9.00 V

c.a.o.

B1

(ii) lost voltage = $E - V$ or $E = I(R + r)$

C1

$$0.82r = 0.59$$

C1

5

internal resistance = 0.720 Ω

A1

(iii) because the battery has to provide more energy/power

B1

[9]

M16.C

[1]

M17.B

[1]

M18.A

[1]

M19.A

[1]

M20.C

[1]

M21.D

[1]

M22.B

[1]

M23.C

[1]

M24.B

[1]

M25.A

[1]

M26.C

[1]