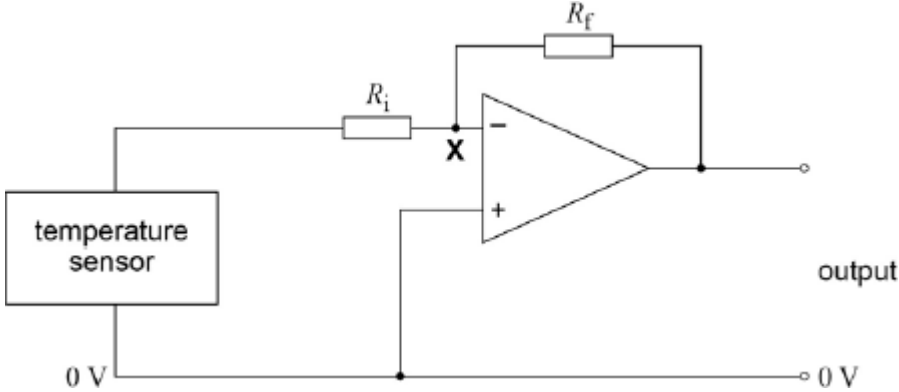


**Q1.**Figure 1 shows a circuit that includes an ideal operational amplifier. A student uses this circuit to amplify the signal from the sensor before further processing by the system.

**Figure 1**



(a) Point X in **Figure 1** is said to be a virtual earth.

Explain the meaning of the term virtual earth in this type of circuit.

.....

.....

.....

(2)

(b) The temperature sensor produces a signal that changes by 10 mV for every degree Celsius change in temperature. The signal is 0 mV when the temperature of the sensor is 0 °C

The value of  $R_i$  is 22 k $\Omega$  and the value of  $R_f$  is 270 k $\Omega$ .

Calculate the output voltage  $V_{OUT}$  of the circuit in **Figure 1** when the sensor is at a temperature of 50 °C.

$V_{OUT} = \dots\dots\dots V$

(2)

- (c) The circuit is powered by a  $-15\text{ V} - 0 - +15\text{ V}$  supply. Explain why this circuit will not detect temperatures above  $122\text{ }^\circ\text{C}$ .

.....

.....


.....

.....

(2)

- (d) A student suggests a modification to the circuit in **Figure 1** to form a difference amplifier circuit for a thermostat. The modified circuit is shown in **Figure 2**.

**Figure 2**

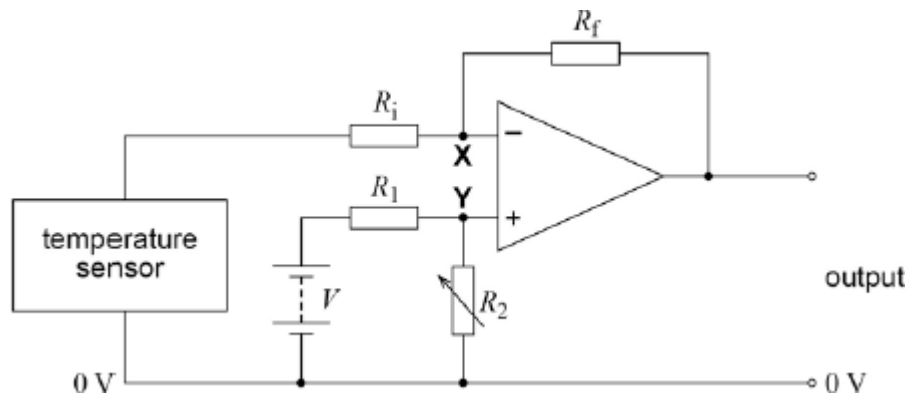

The output controls a circuit that switches the heater off when the output is positive.

Explain how this circuit operates so that the heater switches off when the temperature reaches a pre-determined level.

.....

.....

.....


.....

.....

.....

(3)  
(Total 9 marks)

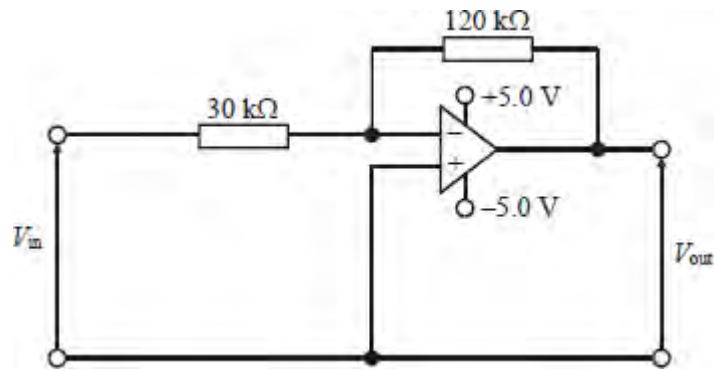**Q2.** The diagram below shows an op-amp used in an amplifier circuit.



(a) Name the type of amplifier circuit shown. ....

(1)

(b) Calculate the output voltage  $V_{out}$  when the input voltage  $V_{in} = 0.50 \text{ V}$ .

.....  
 .....

(2)

(c) The input is now connected to a sinusoidal source of rms output 2.0 V and frequency 50 Hz.


(i) Calculate the peak input voltage.

.....  
 .....

(ii) On the axes below draw a trace showing **two** cycles of the input signal and label it **A**.

On the same axes, draw the **two** corresponding cycles of the output signal and label it **B**.

Add suitable scales to the axes.

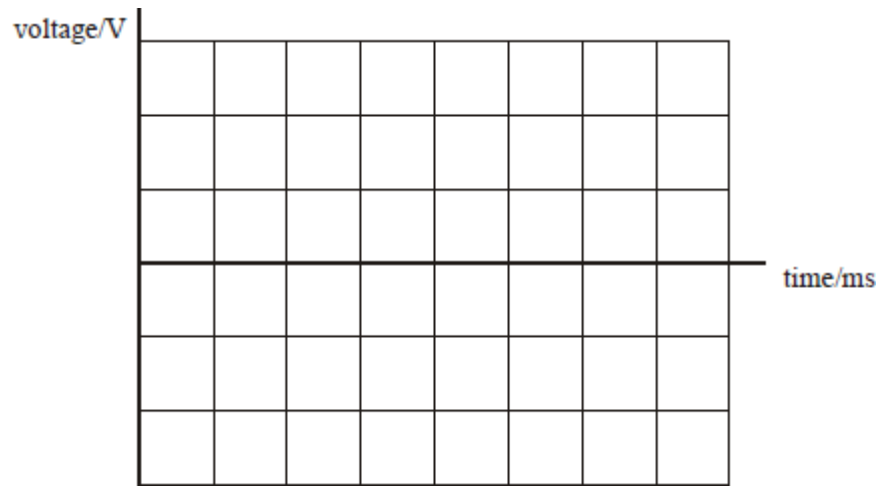

(6)  
(Total 9 marks)