



A-Level Physics

Analogue Signal Processing

Mark Scheme

Time available: 59 minutes

Marks available: 57 marks

www.accesstuition.com

Mark schemes

1.

- (a) Numerical value for capacitor = 6.9 pF ✓

Substitution of values into formula alone – not sufficient for mark.

1

- (b) Y and X most suitable / (W and Z out of range) ✓

Y better than X as value falls within centre of range. ✓

implied choice – 1 mark

reason – 1 mark

2

- (c) Evidence of reading at 0.7 V_{\max} (350 mV) ✓

Bandwidth 20 kHz ✓ Allow range (19–21 kHz)

1 mark only for:

Evidence of reading at 0.5 V_{\max} (250 mV)

Bandwidth 25 kHz ✓ Allow range (24–26 kHz)

2

- (d) $Q = f_0 / f_B = 198 \text{ kHz} / 20 \text{ kHz} = 9.9$ ✓

Allow ecf from (c)

1

- (e) **Either:**

Listener hears overlapping stations - due to increase in bandwidth. ✓

Or

Listener hears station more faintly - due to energy loss / wider energy distribution ✓

*Accept S/N argument as weaker stations become more prominent
and can be considered as noise.*

1

[7]

2.

- (a) $f = 1 / (2\pi \sqrt{LC})$

$$C = 1 / f^2 4\pi^2 L$$

$$C = 1 / (910 \times 10^3)^2 \times 4 \times \pi^2 \times 1.1 \times 10^{-3}$$


$$C = 27.8 \text{ pF (accept 28pF)}$$

Formula with correct substitution / evidence of correct working

Answer

1

1

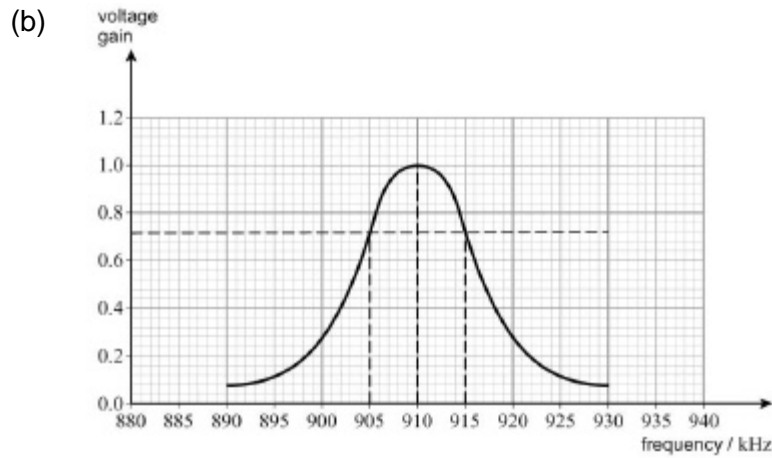

General shape around f_0 and to max of 1.0 on relative voltage gain axis

1

*10 kHz bandwidth
at 0.71 gain*

1

Frequencies (905 – 910 – 915) kHz (identified / used)

1

(c) Smaller Q factor leads to:

(Any **two** from)

(i) Broader bandwidth

(ii) More noise / (hiss) detected

(iii) Less selectivity

(iv) More susceptible to crosstalk from neighbouring stations on the frequency spectrum.

(v) Less gain due to energy loss / loss of signal detail

2

[7]

3.

(a) (i) Log graph enables a wide range of values to be displayed on the same axis.


Allow – (enables values to be displayed as straight line)

1

(ii) 7 lux

1

(b)

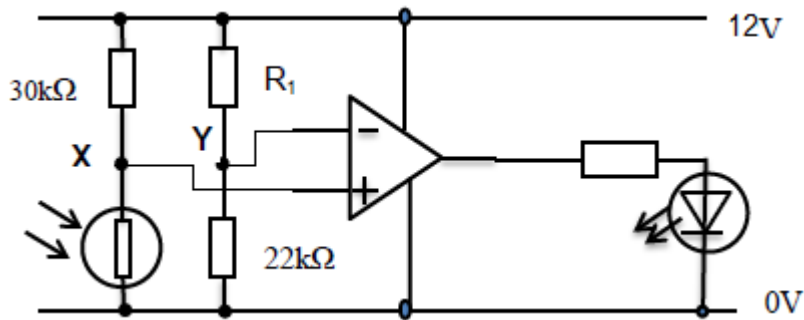

1 mark for connections correct way round

1

(c) (i) $60 \text{ k}\Omega / (60 \text{ k}\Omega + 30 \text{ k}\Omega) \times 12 \text{ V} = 8 \text{ V}$

Working - 1

Answer - 1

2

(ii) $R_1 = 11 \text{ k}\Omega$ to give same value at Y as switching voltage at X (2:1 ratio) (No ecf on value)

Reason / calculation - 1

Answer - 1

2

(d) The op-amp is not ideal and will saturate above 0V

Saturation - 1

Need to drop voltage

Voltage drop - 1

Acceptable method

Method - 1

3

(Total 10 marks)

4.


(a) Feedback resistor from output to -ve input
Correct inverting or non-inverting amplifier circuit
For inverting, 4.7kΩ and 470kΩ in the correct place
For non-inverting, 4.7Ω input resistor AND two resistors in ratio of 99 / 100

4

(b) Formula
120mV
0.12V
(No unit error if obvious)

2

(c)

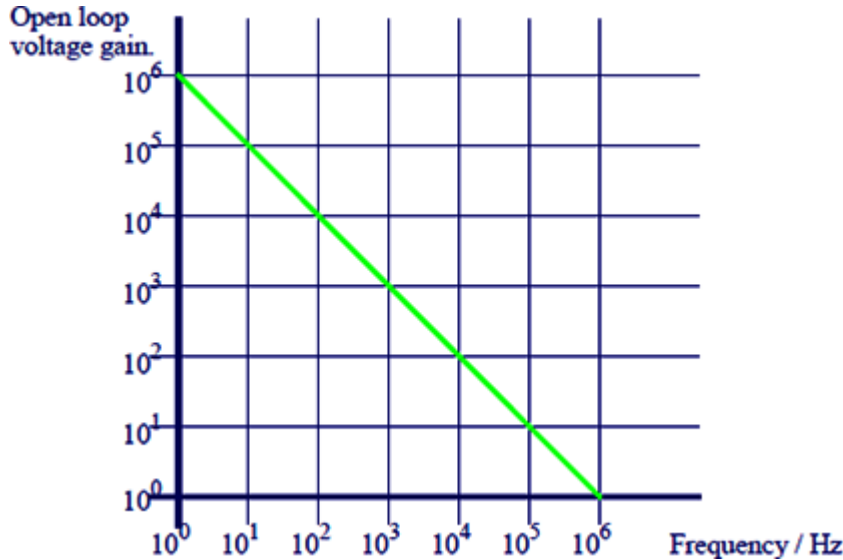

Positive gradient = no marks
 Correct intercept on vertical axis
 Correct intercept on horizontal axis
 Straight line joining

3

(d) (No possible ecf from (c))
 Calculation
 10kHz

2

[11]

5.

(a) use of $f = 1 / 2\pi\sqrt{LC}$, change subject to $L = 1 / 4\pi^2f^2C$
 substitute values, calculation, leading to $6.9\mu\text{H}$ ✓✓✓✓

4

(b) use of $\lambda = c / f$, substitute values leading to 22.1m ✓
 dipole = 11.05m ✓
 too large for desk operation ✓

3

(c) $13.56 / 0.1 = 136$ ✓ (could be rounded down to 135)

1

(d) $1\text{KB} = 8192$ bits (allow 8000) ✓
 $8192 / 100000 = 0.082\text{s}$
 (or allow values based on 8000, 0.08s) regardless of these variations, time to download centres on 80ms ✓

2

[10]

6.

(a) Two input resistors to the inverting input ✓,
 feedback resistor to the inverting input from the output ✓,
 non-inverting input to 0V ✓

3

- (b) All resistors the same value ✓,
 $1\text{k}\Omega < R < 4\text{M}\Omega$ ✓ 2
- (c) Two input resistors, one to each op-amp input ✓,
 feedback resistor to the inverting input from the output ✓,
 resistor from non-inverting input to 0V ✓ 3
- (d) All resistors the same value ✓,
 $1\text{k}\Omega < R < 4\text{M}\Omega$ ✓ 2
- (e) $(L + R) + (L - R) = 2L$ ✓,
 $(L + R) - (L - R) = 2R$ ✓
or equivalent by diagram or description 2

[12]