



# **A-Level Physics**

## **Basics of Electricity**

### **Mark Scheme**

**Time available: 59 minutes**

**Marks available: 49 marks**

**[www.accesstuition.com](http://www.accesstuition.com)**

## Mark schemes

1.

(a) **Method 1:**

Attempts to determine area under curve / by counting squares <sub>1</sub>✓

Multiplies their (total) area (or charge) by 24 (V) <sub>2</sub>✓

240 (J) <sub>3</sub>✓

*Allow POT error on area of square in <sub>1</sub>✓ and <sub>2</sub>✓*

*Evidence seen by calculations **or** from counting squares **or** from division of area into **at least two** recognisable geometrical shapes (triangles, rectangles, trapezia)*

*answer in range 220 J to 264 J*

**Method 2:**

Attempt to determine average current (over first 200 ms in range 45 A to 55 A) <sub>1</sub>✓

Use of  $E = I \times V \times t$  <sub>2</sub>✓

240 (J) <sub>3</sub>✓

*Substitutes current value (or  $\Delta$  current) with  $t = 200$  ms and  $V = 24$  V. Condone POT*

*Allow as two stage  $Q=It$  and  $E=QV$*

*Or  $P = VI$  **and**  $E = Pt$*

*answer in range 220 J to 264 J*

3

(b) (KE (gained) =) 65(.0) (J) **or**

(PE (gained) =) 58(.3) (J) <sub>1</sub>✓

Use of efficiency =  $\frac{\text{an output energy}}{\text{ans from part 04.1}}$

*Allow output energy = 65 /58/ 120 /123 or candidate ke + pe*

**or** (total output = 65 + 58 =) 123 (J) <sub>2</sub>✓

*Allow ecf from (a) for all 3 marks.*

(Efficiency =) 0.51 or 51% <sub>3</sub>✓

*Answer to at least 2 sf. Range is 0.467 to 0.56 (46.7 % to 56 %)*

3

- (c) Heating occurs / temperature increases when there is a current (in the thermistor) (due to  $I^2R$ ) <sub>1</sub>✓

(When the temperature increases) the resistance of thermistor decreases (whereas fixed resistor remains high) <sub>2</sub>✓

(Lower resistance from thermistor means) less wasted power <sub>3</sub>✓

OR

(Lower resistance from thermistor means) more pd dropped across the motor (less wasted voltage) <sub>3</sub>✓

*Alternatively: (Lower resistance from the thermistor means) less voltage drop across thermistor <sub>3</sub>✓*

3

[9]

2.

- (a) The current through a conductor between two points is directly proportional to the potential difference across the two points

(provided the temperature remains constant) ✓

*Or ratio of voltage / current is constant*

1

- (b) 75 (mA) ✓

1

- (c) **MAX 4**

voltmeter position is incorrect because it is across the cell✓

voltmeter should be connected across the putty✓

the 10  $\Omega$  resistor is not suitable to control the current✓

because its resistance is only half that of the putty✓

pd range is 1.0 to 1.5 V, this is insufficient for experiment✓

MAX 4

- (d) Substitution of  $V = A \times l$  into  $\rho = \frac{R \times A}{l}$  ✓

(leading to  $\rho = \frac{RV}{l^2}$ )

*Complete argument needed*

1

(e)  $V = 60 \times 10^{-3} \times \pi \times (10 \times 10^{-3})^2$

$(= 1.88 \times 10^{-5} \text{ m}^3) \checkmark$

$\rho = 20 \times 1.88 \times 10^{-5} / (60 \times 10^{-3})^2$

$= 0.10 \checkmark \Omega\text{m} \checkmark$

*Will not gain this mark only if POT error correctly followed through.*

*Stand alone unit mark*

3

[10]

3.

(a)  $I_3 = I_1 + I_2 \checkmark$

1

(b) 10 V  $\checkmark$

1

(c)  $I_2 = (12 - 10) / 10 \checkmark$

*Allow ce for 10 V*

1

$= 0.2 \text{ A} \checkmark$

*The first mark is for the pd*

*The second is for the final answer*

1

(d) pd across  $R_2$  increases

As  $R_1$  increases, pd across  $R_1$  increases as  $\text{pd} = I_1 R_1 \checkmark$

*First mark is for identifying that pd across  $R_1$  increases (from zero).*

1

$\text{pd across } R_3 = 10 \text{ V} - \text{pd across } R_1$

Therefore pd across  $R_3$  decreases  $\checkmark$

*Second mark is for identifying that pd across  $R_3$  must decrease*

1

$\text{pd across } R_2 = 12 - \text{pd across } R_3$

Therefore pd across  $R_2$  increases  $\checkmark$

*Third mark is for identifying that this means pd across  $R_2$  must increase*

1

[7]

4.

(a) Correct substitution into  $P=VI$

1.74 (A)

2

- (b) (i) Correct substitution into  $R=V/I$  or  $V^2/P$  or  $P/I^2$   
 264 ( $\Omega$ )  
*Allow correct use of parallel resistor equation* 2
- (ii) Use of  $1/R_T = 1/R_1 + 1/R_2$  or  $R = V^2/P$   
 65 (66.1) ( $\Omega$ ) 2
- (iii)  $A = \pi(1.5 \times 10^{-4})^2/4$  or  $\pi(7.5 \times 10^{-5})^2$  or  $1.767 \times 10^{-8}$  ( $m^2$ )  
 Substitution into  $l=RA/\rho$  with their area  
 4.2 (4.18) (m)  
*2 marks for 17 (m), using of d instead of r* 3
- (c) Resistivity / resistance increases with increasing temperature  
 (Lattice) ions vibrate with greater amplitude  
 Rate of movement of charge carriers / electrons (along wire)  
 reduced (for given pd)  
*ORA*  
*Condone atoms for ions.*  
*Accept "vibrate more".*  
*Accept more frequent collisions occur between electrons and ions*  
*owtte* 3
- (d)  $2.9 \times 10^{-3}/447$  or  $2.9 \times 10^{-3}/174$  seen  
 $6.5$  ( $6.49$ )  $\times 10^{-6}$  (m)  
 Correct answer given to 2 sig fig  
*Condone use of 174 for T for C1 and B1 marks*  
*Allow 3 sig fig answer if  $2.90 \times 10^{-3}$  used* 3

[15]

5.

- (a) emf is the work done / energy transferred by a voltage source / battery / cell  $\checkmark$  per unit  
 charge $\checkmark$   
 OR  
 electrical energy transferred / converted / delivered / produced $\checkmark$   
 per unit charge $\checkmark$   
 OR  
 pd across terminals when no current flowing / open circuit $\checkmark\checkmark$   
*not in battery*  
*accept word equation OR symbol equation with symbols defined if*  
*done then must explain energy / work in equation for first mark* 2
- (b) (i) by altering the (variable) resistor $\checkmark$  1

(ii) reference to correct internal resistance✓

*e.g. resistance of potato (cell)*

terminal pd = emf – pd across internal resistance / lost volts✓

pd / lost volts increases as current increases OR as (variable)

resistance decreases greater proportion / share of emf across internal resistance✓

*accept voltage for pd*

3

(iii) draws best fit straight line and attempts to use gradient✓

uses triangle with base at least 6 cm✓

value in range 2600 – 2800 ( $\Omega$ )✓

3

*stand-alone last mark*

(c) total emf is above 1.6 V✓

but will not work as current not high enough / less than 20 mA✓

2

[11]