



**A-Level Physics**  
**Discrete Semiconductor**  
**Devices**  
**Mark Scheme**

**Time available: 73 minutes**  
**Marks available: 42 marks**

**[www.accesstuition.com](http://www.accesstuition.com)**

## Mark schemes

1.

- (a) Silicon dioxide layer ✓

*Accept Silicon dioxide*

1

- (b)

drain

gate

source

1

- (c) For lamp  $P = I^2 R$

$$I = \sqrt{(P/R)} = \sqrt{(0.65 \text{ W} / 154 \Omega)} = 65 \text{ mA} \checkmark_1$$

*Must use  $P = I^2 R$*

This leads to a voltage across the lamp of approx 10 V and a  $V_{DS}$  of approx 2 V

Read from graph to give  $V_{GS} = 3.4 \text{ V} \checkmark_2$

*Accept a  $V_{GS}$  range of 3.3 V to 3.5 V*

2

- (d) Current consumption on stand-by:  $8.5 \times 10^9 \times 10 \times 10^{-9} = 85 \text{ A} \checkmark_1$

*Makes a meaningful calculation (one which can lead to a conclusion) using data for the CPU.*

Battery life:  $3600 \text{ C} \times 3.110 = 1.12 \times 10^4 \text{ C} \checkmark_2$

*Makes a meaningful calculation (one which can lead to a conclusion) using data for battery.*

Use  $1.12 \times 10^4 = 85 \times t$

Gives  $t = 131.8$  seconds (accept 132 seconds OR just over 2 mins) which is much less than 12 hours  $\checkmark_3$

*Uses the value of  $t$  to reach a valid conclusion*

OR

*Uses the values of the currents from the CPU and battery to reach a valid conclusion*

3

[7]

2.

- (a) Photoconductive mode

*Accept 'reverse bias'*

1

- (b) Dark currents will become a source of noise – need to keep S:N as high as possible  
OWTTE

OR

Need to have a large difference in signal when detector is in light and dark ✓

*Must include idea of 'noise'*

OR

*Must include concept of large signal change to represent digital signal*

1

- (c) At 850 nm,  $R_\lambda = 0.50 \text{ A/W}$  ✓

*Reading from graph*

*Allow 0.49 A/W to 0.51 A/W*

$$\text{Using } R_\lambda = \frac{I_p}{P} \quad I_p = R_\lambda \times P \quad 0.50 \times 4 \times 10^{-6} = 2 \mu\text{A} \quad \checkmark \quad \text{ecf}$$


$$V_{\text{out}} = I_p \times R = 2 \mu\text{A} \times 560 \text{ k}\Omega = +1.12 \text{ V} \quad \checkmark$$

*Accept voltage in range of 1.10 V to 1.14 V*

*Accept value without + sign*

3

- (d)

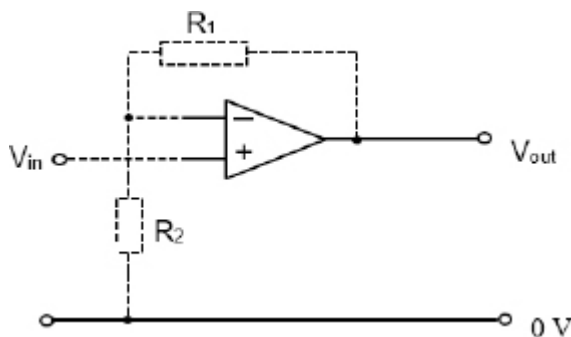

*Correct configuration of  $R_1$  and  $R_2$  ✓*

*$R_1 : R_2$  ratio 3 : 1 in suggested range ✓*

*Label the input point which must have a direct connection to the non-inverting input ✓*

*One mark only*

*An inverting op amp configuration with a voltage gain  $-4$ .*

3

[8]

3.

(a) **With the north pole facing the sensor:**

Higher sensitivity/larger gradient ✓ over very short range ✓

Some ambiguity in liquid level due to peak in graph – (more than one level referenced to a single output reading) ✓

OR

**With the south pole facing the sensor:**

Less sensitivity/smaller gradient ✓ but covers a larger range ✓

No ambiguity in liquid level – (each level produces a discrete output up to saturation) ✓

*Mark awarded for each compared point*

3

(b) 2.4 divisions @ 5 ms / div = 12 ms

Periodic time  $T = 12 \text{ ms} \times 3 = 36 \text{ ms}$  ✓

Or

7.2 divisions @ 5 ms / div = 36 ms

$f = 1 / T$ ;  $f = 1 / 36 \text{ ms}$ ; 27.8 rev / sec ✓

27 full revolutions in one second ✓

*One mark for appropriate reading from graph to produce periodic time (T).*

*One mark for frequency using their (T).*

*One mark for rounding down*

3

[6]

4.

(a) +ve knee develops at 0.7 V and does not exceed 1.5 V at 30 mA ✓

–ve knee develops at 5.1 V; 5 mA with near vertical drop. Does not exceed – 5.5 V at –30 mA ✓

2

(b) Zener diode provides a reference voltage for non-inverting input ✓

Or

Zener diode provides a stabilised voltage for non-inverting input ✓

*Accept combination of the two statements*

1

(c)  $I = V/R = 3.9 \text{ V} / 100 \Omega = 39 \text{ mA}$

This is larger than the minimum current to make Zener diode work so the resistor value is fine. ✓

$$P = I^2 R = (39 \times 10^{-3})^2 \times 100 = 0.152 \text{ watts}$$

This is greater than the power rating for the resistor, so is not a suitable power rating for the resistor ✓

*Ecf from value of I*

2

(d) The reference voltage at the non-inverting input is now smaller ✓

This will cause the output **W** to switch at a lower light intensity than before ✓

2

(e)  $Q = (\overline{X+Y}) \cdot W$  ✓

*Accept transformations eg*

$$Q = \overline{X} \cdot (\overline{Y+W})$$

$$Q = \overline{X} \cdot Y \cdot \overline{W}$$

1

(f) MOSFET has large input impedance

OR

MOSFET causes no loading of the logic gate output. ✓

1

[9]

5.

(a) High input resistance ✓

low / no energy consumption when in the ON and OFF states ✓

OR

No input current / control by pd only.

2

(b) Prevents static charge building up on gate (-source capacitor) ✓

Makes gate voltage 0 V when no water / nothing between probes ✓

2

(c) Identifies or attempts to use potential divider equation ✓

$$2.4 = 12 \times 1 / (R_{\text{probes}} + 1) \text{ leading to } R_{\text{probes}} = 9.6 / 2.4 = 4 \text{ M}\Omega \text{ ✓}$$

2

[6]

6.

(a) Photoconductive (accept reverse bias)

1

(b)

	Tick (✓) if correct
Non-inverting amplifier	
Comparator	✓
Summing amplifier	
Difference amplifier	

1

(c) Light level ~ 1000 lux +/- 10%

1

(d)  $V_x = IR$ ;  $V_x = 100 \mu\text{A} \times 20 \text{ k}\Omega = 2 \text{ V}$

1

(e) Rule that if  $V_- > V_+$  then  $V_{\text{out}}$  is 0 V (low)

1

Voltage drop across LED so LED is ON

*Do not allow LED is ON if supported by incorrect reason*

1

**[6]**