



A-Level Physics

Electricity (Multiple Choice)

Question Paper

Time available: 20 minutes

Marks available: 20 marks

www.accesstuition.com

1. As the temperature of a copper wire increases, its resistance

- A remains constant.
- B increases.
- C decreases.
- D remains constant at first and then decreases.

(Total 1 mark)


2. A $12\ \Omega$ resistor is connected across the terminals of a cell that has an emf of $2.0\ \text{V}$ and an internal resistance of $4.0\ \Omega$.

What is the terminal pd?

- A $0.50\ \text{V}$
- B $0.75\ \text{V}$
- C $1.30\ \text{V}$
- D $1.50\ \text{V}$

(Total 1 mark)

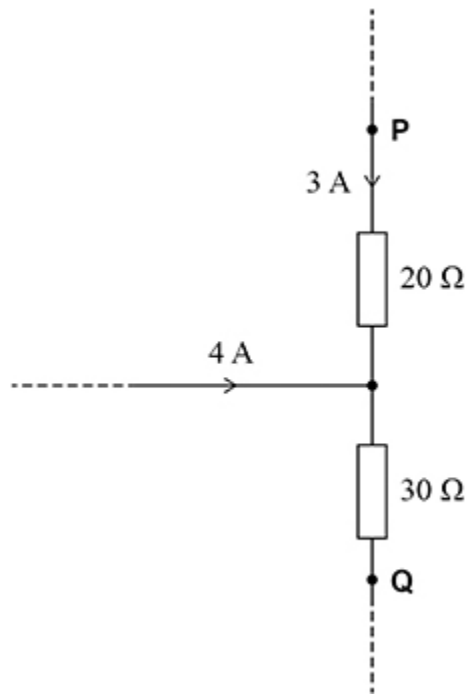3. The diagram shows the currents in part of a circuit.




What is the potential difference between points **P** and **Q**?

- A $60\ \text{V}$
- B $70\ \text{V}$
- C $180\ \text{V}$
- D $270\ \text{V}$

(Total 1 mark)

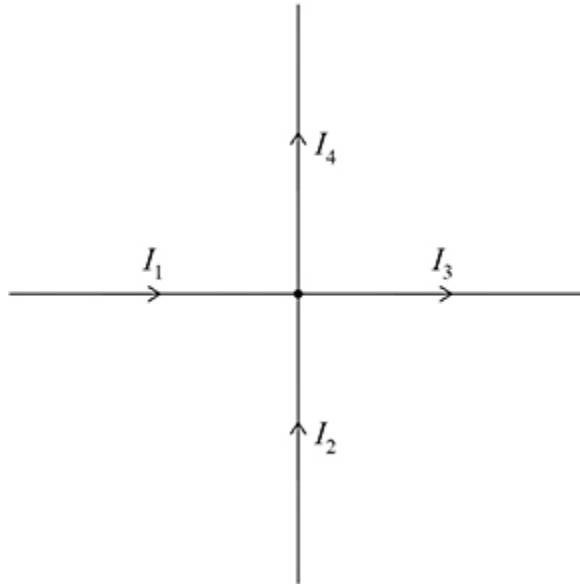4. The currents in the four wires obey the relationship $I_1 + I_2 + I_3 + I_4 = 0$



This relationship is an expression of the law of conservation of

- A charge.
- B energy.
- C potential difference.
- D power.

(Total 1 mark)

5. Which value of resistance **cannot** be made by combining three $10\ \Omega$ resistors?

- A $3.3\ \Omega$
- B $6.7\ \Omega$
- C $15\ \Omega$
- D $25\ \Omega$


(Total 1 mark)

6. The current in a metallic conductor is 1.5 mA.
How many electrons pass a point in the conductor in two minutes?

- A 1.1×10^{18}
- B 1.9×10^{19}
- C 1.4×10^{20}
- D 2.0×10^{29}

(Total 1 mark)

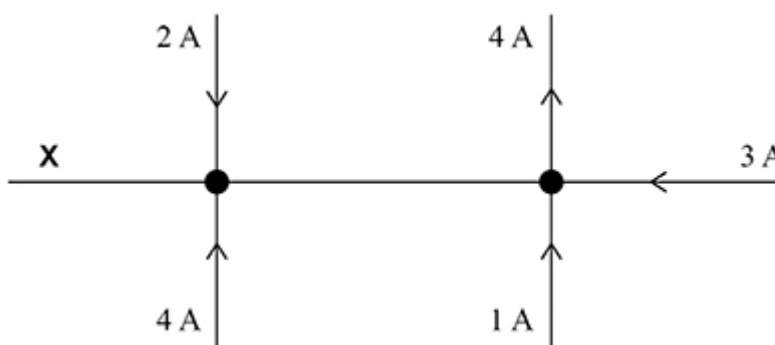7. The diagram shows the currents in a set of wires.




What is the magnitude of the current at **X**?

- A zero
- B 2 A
- C 3 A
- D 6 A

(Total 1 mark)

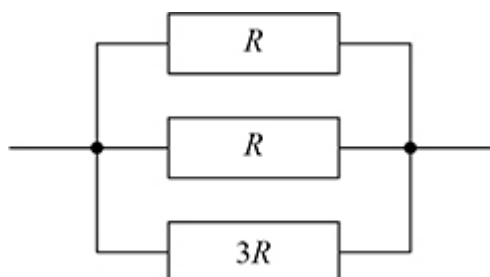8. Resistors of resistance R , R and $3R$ are connected as shown.



What is the resistance of the arrangement?

- A $\frac{3R}{7}$
- B $\frac{7R}{3}$
- C $\frac{5R}{6}$
- D $\frac{6R}{5}$

(Total 1 mark)

9.


Superconductors are used to

- A increase the strength of electricity cables.
- B make light dependent resistors.
- C produce strong magnetic fields.
- D increase the rate of heat energy transfer.

(Total 1 mark)

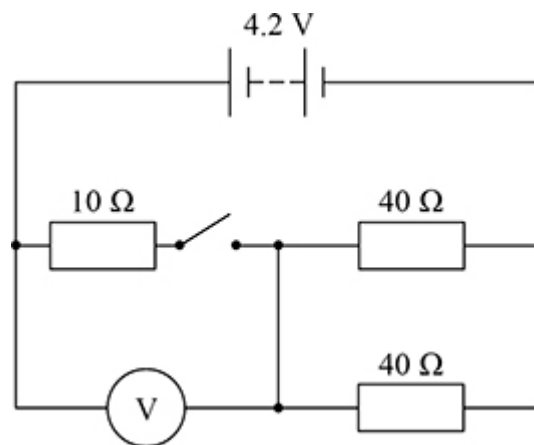10.

The battery in this circuit has an emf of 4.2 V and negligible internal resistance.




What are the readings on the voltmeter when the switch is open (off) and when the switch is closed (on)?

	Open	Closed	
A	0 V	2.1 V	<input type="radio"/>
B	4.2 V	2.1 V	<input type="radio"/>
C	0 V	1.4 V	<input type="radio"/>
D	4.2 V	1.4 V	<input type="radio"/>

(Total 1 mark)

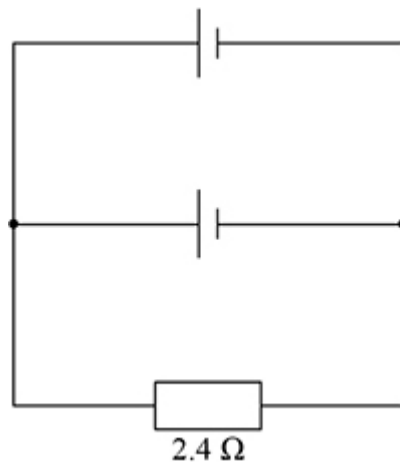11.

Two identical batteries each of emf 1.5 V and internal resistance 1.6Ω are connected in parallel. A 2.4Ω resistor is connected in parallel with this combination.



What is the current in the 2.4Ω resistor?


- A** 0.38 A
- B** 0.47 A
- C** 0.75 A
- D** 0.94 A

(Total 1 mark)

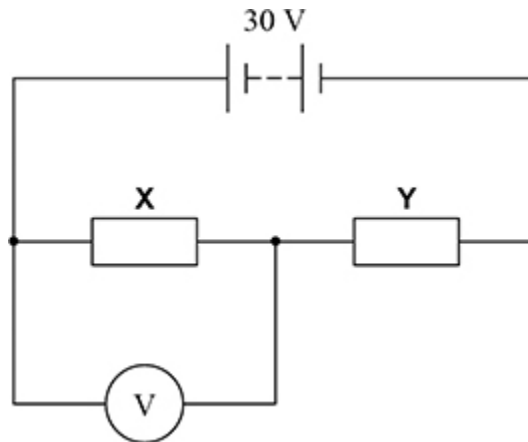12.

Two resistors **X** and **Y** are connected in series with a power supply of emf 30 V and negligible internal resistance.

The resistors are made from wire of the same material. The wires have the same length. **X** uses wire of diameter d and **Y** uses wire of diameter $2d$.



What is the reading on the voltmeter?

A 10 V

B 15 V

C 20 V

D 24 V

(Total 1 mark)

13.

The capacity of a portable charger is rated in ampere hours (A h). A charger of capacity 1 A h can provide 1 A for 1 hour at its working voltage.

One charger has a capacity of 1800 mA h at a working voltage of 3.7 V.

What is the energy stored in this charger?

A 6.5 kJ

B 24 kJ

C 400 kJ

D 24 kJ

(Total 1 mark)

14.

A filament lamp with resistance 12Ω is operated at a power of 36 W .

How much charge flows through the filament lamp during 15 minutes?

A 26 C

B 1.6 kC

C 2.7 kC

D 6.5 kC

(Total 1 mark)

15.

A resistor with resistance R is made from metal wire of resistivity ρ . The length of the wire is L .

What is the diameter of the wire?

A $\sqrt{\frac{2\rho R}{\pi L}}$

B $\sqrt{\frac{2\rho L}{\pi R}}$


C $2\sqrt{\frac{\rho L}{\pi R}}$

D $2\sqrt{\frac{\rho R}{\pi L}}$

(Total 1 mark)

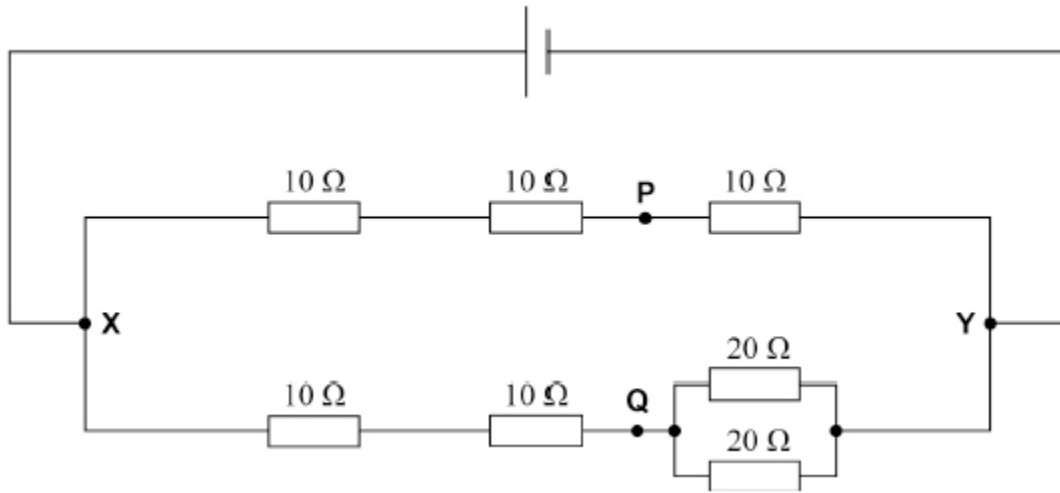16.

The potential difference between points X and Y is V .




What is the potential difference between P and Q?

- A zero
- B $\frac{V}{3}$
- C $\frac{V}{2}$
- D $\frac{2V}{3}$

(Total 1 mark)

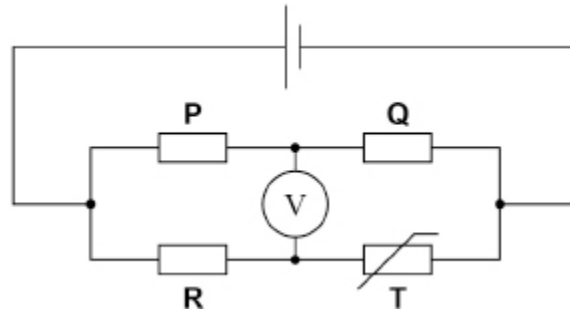17.

In the circuit below, the voltmeter reading is zero.



When the temperature of the thermistor **T** is increased, the voltmeter reading changes.


Which change to the circuit will restore the voltmeter to zero?

- A a reduction in the emf of the cell
- B a reduction in the resistance of **P**
- C an increase in the resistance of **Q**
- D a reduction in the resistance of **R**

(Total 1 mark)

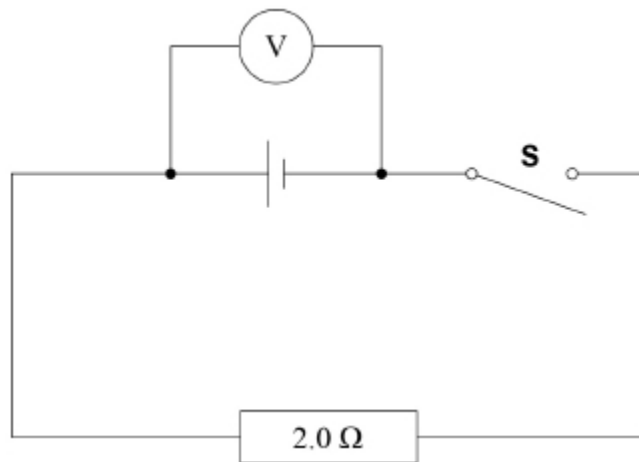18.

The reading on the voltmeter halves when switch **S** is closed.



What is the internal resistance of the cell?

A 0.50 Ω

B 1.0 Ω

C 2.0 Ω


D 4.0 Ω

(Total 1 mark)

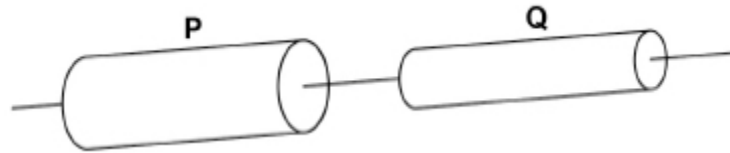19.

Two cylindrical wires **P** and **Q** are of equal length and made of the same material. The diameter of **P** is greater than that of **Q**.

P and **Q** are connected in series and the ends of this arrangement are connected to a power supply.




Which two quantities are the same for **P** and **Q**?

A	potential difference across wire	resistivity	<input type="checkbox"/>
B	resistivity	current	<input type="checkbox"/>
C	current	resistance	<input type="checkbox"/>
D	resistance	potential difference across wire	<input type="checkbox"/>

(Total 1 mark)

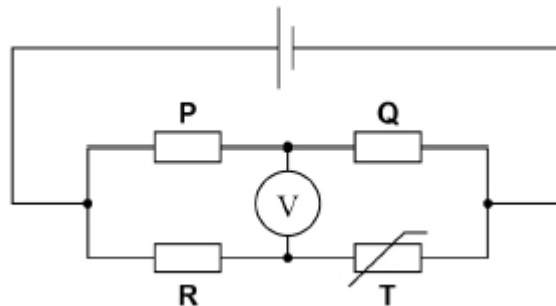20.

In the circuit below, the initial voltmeter reading is zero.



The temperature of the negative temperature coefficient thermistor **T** is then increased.

Which change to the circuit could restore the voltmeter reading to zero?

A Decreasing the resistance of **R**.

B Increasing the resistance of **R**.

C Decreasing the resistance of **P**.

D Increasing the resistance of **Q**.

(Total 1 mark)