



A-Level Physics

Electromotive Force

Mark Scheme

Time available: 72 minutes

Marks available: 55 marks

www.accesstuition.com

Mark schemes

1.

- (a) Use of power equation

OR

Power equation and $V = IR$

To give $R = 8.5 \text{ } (\Omega) \checkmark$

1

- (b) Calculation of parallel pair resistance = $5.0 \text{ } \Omega \checkmark$

Calculation of circuit current = $6.2 / 5.0 = 1.24 \text{ A}$

emf = terminal pd + $Ir = 6.2 + (1.24 \times 2.5) \checkmark$

9.3 V \checkmark

Allow ecf from (a)

Allow alternative methods

3

- (c) $A = \pi (d / 2)^2 = 2.84 \times 10^{-8} \checkmark$

Use of resistivity equation = $RA/l \checkmark$

To give $5.0 \times 10^{-8} \checkmark$

Allow POT error in MP1

And MP2

3

- (d) Resistance increases \checkmark

Reduces current through lamp

Lamp dimmer \checkmark

2

- (e) (Resistance increases)

Reduces current in battery \checkmark

Reduces lost volts and increases terminal pd

lamp brighter. \checkmark

Give 1 max for arguments dealing with initial dimming of bulb when wire attached.

2

[11]

2.

- (a) Work done in moving 1 C of charge through the cell ✓
1.5 J of work is done in moving 1 C of charge through the cell ✓

OR

Amount of energy converted from other forms to electrical energy per 1 C of charge ✓

1.5 J of energy converted from other forms to electrical energy per unit charge (passing across the emf) ✓

OR

Work done in moving 1 C of charge (whole way) round circuit ✓

1.5 J of work is done in moving 1 C of charge the (whole way) round circuit ✓

2nd marking point obtains both marks

Max 1 mark available for the following:

The emf is the terminal pd when there is no current in the cell (and this equals 1.5 V)

1.5 J of energy per 1 C of charge.

Allow a statement of Kirchhoff's 2nd law for 1 mark. Where the law is in symbol form, the meaning of the symbols must be stated. Need a clear communication of internal and external resistances.

2

- (b) $P = VI$

And

$(P) = 0.465 \text{ (W)} \checkmark$

Seen to more than 2 sf with supporting equation with subject seen in working

1

- (c) Use of appropriate power equation to determine wasted power
or
power dissipated in **R** = total power – their wasted power ✓

(*P* =) 0.40 W ✓

Alternative for 1 mark:

Use of $I = \frac{\epsilon}{R+r}$

Or

pd across *R* = 1.5 – 0.65 x 0.31

or

pd across *R* = 1.2985 (V)

or

total resistance = 1.5/ 0.31

or

total resistance = 4.839 (Ω)

or *R* = 4.2 (Ω)

or $P = I^2 \times \text{their } R$

or

$P = \frac{V^2}{R}$ using their *V* and *R* ✓

2

- (d) Use of $E = P t$

or $E = VI t$

Or

$E = QV$ and $Q = It$ ✓

Allow use of the equation with their values.

An answer of 3.5×10^4 is worth 1 mark

(*t* =) 3.0(1) x 10⁴ (s) ✓

2

(e) **MAX 3 from (1 to 4) or (5 to 8)**

It is suitable, because:

(1) Current required in lamp = 0.62 A or use of $I = \frac{P}{V}$ seen

(2) Resistance of lamp = 2.11 Ω or use of $R = \frac{V^2}{P}$ seen ✓

(3) current in each cell = 0.31 A ✓

(4) lost volts = 0.2 V

or

lost volts = 0.65 x 0.31 ✓

Check the diagram in part (e)

*Must have the **correct conclusion to award 4 marks.***

Conclusion: yes, terminal pd = 1.5 – 0.2 seen

or

terminal pd = 1.5 – 0.65 x 0.4 / 1.3 ✓

OR

(5) total internal resistance = 0.325 Ω ✓

(6) total resistance in circuit = 2.44 Ω ✓

(7) Resistance of lamp = 2.11 Ω ✓

(8) pd splits in ratio of 0.325:2.11 ✓

Conclusion: yes, pd across lamp is $\frac{2.11 \times 1.5}{2.44}$ (= 1.3 V) seen ✓

Allow max 3 from a combination of two route [(2) and (7) worth total of 1 mark]

(e) (Cells must be added) in parallel ✓

Because:

more energy stored in the bank of cells / less power from each cell ✓

without increasing the voltage across the bulb (above 1.5 V)

or

without increasing the terminal pd (above 1.5V) ✓

Must link the cells being added in parallel to one or both reason to gain three marks.

Alternative:

- *In parallel*
- *Current shared by cells*
- *Takes longer to convert the energy stored in each cell.*

Alternative:

- *In parallel*
- *Less internal resistance*
- *Less power / energy wasted*

Cells in series statement means no marks can be obtained.

3

[14]

3.

(a) (i) Voltmeter across terminals with nothing else connected to battery / no additional load.
✓

1

(ii) This will give zero / virtually no current ✓

1

(b) (i) $\frac{VI}{\epsilon I}$

Answer must clearly show power: ϵI and VI , with I cancelling out to give formula stated in the question ✓

1

(ii) Voltmeter connected across cell terminals ✓

Switch open, voltmeter records ϵ

Switch closed, voltmeter records V

Both statements required for mark ✓

Candidates who put the voltmeter in the wrong place can still achieve the second mark providing they give a detailed description which makes it clear that:

To measure emf, the voltmeter should be placed across the cell with the external resistor disconnected

And

To measure V , the voltmeter should be connected across the external resistor when a current is being supplied by the cell

2

(c) Vary external resistor and measure new value of V , for at least 7 different values of external resistor ✓

Precautions - switch off between readings / take repeat readings (to check that emf or internal resistance not changed significantly) ✓

2

(d) Efficiency increases as external resistance increases ✓

Explanation

Efficiency = Power in R / total power generated

$$I^2 R / I^2 (R + r) = R / (R + r)$$

So as R increases the ratio becomes larger or ratio of power in load to power in internal resistance increases ✓

Explanation in terms of V and ϵ is acceptable

2

[9]

4.

(a) mention of pd across internal resistance **or** energy loss in internal resistance **or** $\text{emf} > V$ ✓

pd across internal resistance/lost volts increases with current **or** correct use of equation to demonstrate ✓

2

- (b) (i) y – intercept 1.52 V (± 0.01 V) ✓✓ 1
- (ii) identifies gradient as r or use of equation ✓✓
substitution to find gradient or substitution in equation ✓✓
 $r = 0.45 \pm 0.02 \Omega$ ✓✓ 3
- (c) (i) same intercept ✓✓
double gradient (must go through 1.25, 0.40 ± 1.5 squares) ✓✓ 2
- (ii) same intercept horizontal line ✓✓ 1
- (d) (i) (use of $Q = It$)
 $Q = 0.89 \times 15 = 13$ ✓✓ C ✓✓ 2
- (ii) use of $P = I^2 r$ ✓✓
 $P = 0.89^2 \times 0.45$
 $P = 0.36$ W ✓✓ 2

[13]

5.

- (a) (i) work (done)/energy (supplied) per unit charge (by battery) (1)
(or pd across terminals when no current passing through
cell or open circuit) 1
- (ii) when switch is closed a **current flows** (through the battery) (1)
hence a pd/lost volts develops across the internal resistance (1) 2
- (b) (use of $\epsilon = V + Ir$)
 $I = 5.8/10 = 0.58$ (A) (1)
 $6.0 = 5.8 + 0.58r$ (1)
 $r = 0.2/0.58 = 0.34$ (Ω) (1) 3

(c) need large current/power to start the car **(1)** (or current too low)

internal resistance limits the current/wastes power(or energy)/reduces terminal pd/increases lost volts **(1)**

2

[8]