



# **A-Level Physics**

## **Potential Dividers**

### **Mark Scheme**

**Time available: 77 minutes**

**Marks available: 58 marks**

**[www.accesstuition.com](http://www.accesstuition.com)**

## Mark schemes

1.

- (a) Use of

$$V_0 = \frac{R_1}{R_1 + R_2} \times V_{in}$$

**OR**

$$V_1 : V_2 = R_1 : R_2 \checkmark$$

$$(R =) 1.7 (\Omega) \checkmark$$

*Alternative MP1:*

*pd across the variable resistor = 11.25 V*

**OR**

*current = 0.45 A*

2

- (b) use of  $V = IR \checkmark$

$$(R =) 4.7 (\Omega) \checkmark$$

2

- (c) Temperature increases so resistance increases  $\checkmark$

Vibration of the lattice ions increases (with temperature)  $\checkmark$

More collisions between the (conduction) electrons and the lattice ions (at higher temperature)  $\checkmark$

3

- (d) use of  $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} \checkmark$

$$(R =) 4.8 (\Omega) \checkmark$$

*Alternative MP1:*

*determines  $I_T$  current in battery ( $I_T = 2.48 \text{ A}$ ) **and** uses  $V = IR$*

2

- (e) use of  $P = \frac{V^2}{R} \checkmark$

$$(P =) 30 \text{ (W)} \checkmark$$

*Ecf from (d)*

2

- (f) Voltage range is wider 0–12 V (in Figure 4's circuit)

**OR**

bulb won't light at lower range so control is unaffected ✓

Efficiency is less because more power dissipated in Figure 4 (for any particular voltage across the lamp compared to this voltage across the lamp in Figure 2) ✓

At any voltage across the lamp there is always 12 V across the resistor in Fig 4 which produces heating whereas only the remaining portion of 12 V is across the resistor in Fig 2 ✓

3

[14]

**2.**

- (a)  $R_{\text{LDR}}$  without light = 300 k $\Omega$  ✓

$$I = \frac{V}{R} = \frac{5}{310 \times 10^3} = 16.1 \times 10^{-6} \text{ A} \checkmark$$

*Allow ecf for their R*

2

- (b)  $V$  with without light =  $IR = 16.1 \times 10^{-6} \times 300 \times 10^3 = 4.84 \text{ V} \checkmark$

*ecf from (a)*

*Allow 92–100 k $\Omega$*

$$\text{With light } V = \left( \frac{93}{93+10} \right) \times 5.0 = 4.51 \text{ V} \checkmark$$

Conclusion and calculate of change in voltage and comparison with 1.25 V ✓

$$4.8 - 4.5 = 0.3 \text{ V so no.}$$

*Allow 1 sf (allow ecf)*

3

[5]

**3.**

- (a) Acceptable line ✓

Condone one failure from the following list

- A. Line straight up to point 8 (expect ruled but condone freehand drawing)
- B. Line shows balance of points on each side of drawn line
- C. Line goes within region of data cross
- D. Appropriate continuous transition between line and curve
- E. Beyond point 12 shows either curve of decreasing gradient OR straight line through points 12 to 15
- F. Thin line and non-variable thickness
- G. Line of acceptable quality, eg not hairy or kinked

**Please annotate on CMI+**

The line must intersect with the cross of the data point.  
 However, condone point 14 or 15 being off line of best fit for a smooth curve.


Condone partially erased and redrawn.

Do not allow double line under any circumstance.

Allow a curve with a slight inflection at point 14

(see example below)

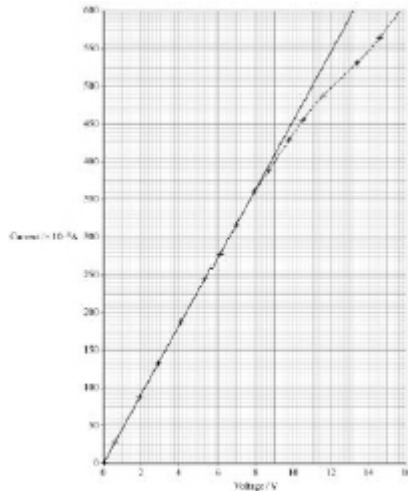Allow a split line where linear section has been extrapolated to the top of the grid e.g.



1

- (b) Circle drawn around data point 9 (8,  $360 \times 10^{-3}$ ) ✓

Condone circle drawn around data point 10 (8.7,  $390 \times 10^{-3}$ )

**provided that** linear section of line intersects with this cross.

1

- (c) Correct read off for voltage from candidate line <sub>1</sub> ✓

This voltage must be within one half-square of actual value.

Correct answer using  $\left( \frac{\text{their } V - 22.2}{\frac{0.55}{22.2}} \right) \times 100$  <sub>2</sub> ✓

Penalise mid-calculation rounding.

Condone missing % sign;

2 or 3 significant figures for answer.

Penalise Physics Error of using gradient of tangent to determine the resistance.

2

(d) circuit **D** is correct <sub>1</sub>✓

circuit **A** is incorrect because the ammeter is not measuring the current in **R**

OR

ammeter is not in series with **R**

OR

the ammeter is measuring the current in the power supply <sub>2</sub>✓

circuit **B** is incorrect because the voltage range (shown in the data) cannot be produced

OR

cannot achieve voltage less than (about) 5 V <sub>3</sub>✓

circuit **C** is incorrect because the voltmeter is not in parallel with **R**

OR

the voltmeter is not measuring the voltage across **R**

OR

the voltmeter reading equals emf minus voltage across **R** <sub>4</sub>✓

*Ignore unclear or incorrect explanation for MP1*

*<sub>2</sub>✓ <sub>3</sub>✓ and <sub>4</sub>✓ are awarded for correct explanations not for a statement that a circuit is incorrect.*

*for <sub>1</sub>✓ accept implied answer that circuit **D** is correct if circuits **A**, **B** and **C** are all stated to be incorrect*

*for <sub>2</sub>✓ any suggestion that in circuit **A** the voltmeter is in the wrong position forfeits the mark*

*Condone circuit **B** is incorrect “because the voltage cannot go down to zero” for <sub>3</sub>✓.*

*Or*

*Condone circuit **B** is incorrect “there is less variation in voltage because the resistors are in series” <sub>3</sub>✓.*

*for weak statements in MP2 and MP4 1 mark for ‘circuit **A** is incorrect because ammeter is in wrong place’ and ‘circuit **C** is incorrect because voltmeter is in the wrong position’*

*If **A** / **B** / **C** is identified as correct then **MAX 2** for two statements that correctly explain why the others are unsuitable.*

*If no other marks awarded: **MAX 1** for “Circuit **B** is correct because the ammeter is series with resistor **R** and the voltmeter is in parallel with **R**”.*

4

[8]

4.

- (a) resistance of lamp B and D =  $3.5^2/4.1 = 3.0$  (2.98)( $\Omega$ ) ✓  
 resistance of lamp A and C =  $6.0^2/6.0 = 6.0$  ( $\Omega$ ) ✓  
 pd across lamp B and lamp D =  $3/9 \times 9.0 = 3.0$  (V) OR pd across lamp A and C = 6.0 (V) ✓  
 hence A and C normal brightness ✓

*Can justify in terms of current i.e. current needed by A and C is 1 A  
 provided resistance values calculated*

*Must have some correct working for conclusion mark*

1  
1  
1  
1

- (b) the pd across new lamp = 0 / E does not light ✓  
 no current in E ✓  
 other lamps are not affected ✓  
 because the current in the lamps/pd across lamps does not change ✓

*2<sup>nd</sup> and 3<sup>rd</sup> marks conditional on 1<sup>st</sup> mark*

1  
1  
1  
(MAX 3)

- (c) in first circuit current in battery =  $9.0/4.5 = 2.0$  A ✓  
 in second circuit current in battery =  $9.0/7 = 1.2857$  A ✓  
 hence current in battery decreases ✓

*Allow ecf from (a)*

*Original current = 2A can come from (a) and score here*

*If say circuit resistance increases so current decreases and no other marks awarded score 1 mark*

1  
1  
1

[10]

5.

- (a) Length of resistance wire =  $50 \times 2 \times 3.14 \times 4 \times 10^{-3} = 1.26$  m ✓  
 or  $50 \times 3.14 \times 8 \times 10^{-3}$

1

Substitution of data in resistance formula

or  $A = \rho L/R$  seen ✓

*ecf for incorrect length from attempt at a calculation*

1

Area of cross section =  $2.1(1) \times 10^{-9}$  (m<sup>2</sup>) ✓

1

- (b) Maximum possible pd across 0.25 k $\Omega$  is 9 V ✓

1

(Max power dissipated) =  $9^2/250 = 0.32$  W so resistor is suitable ✓

1

**OR**

When resistor dissipates maximum power

$$V^2 = 0.36 \times 250 \text{ so max } V = 9.5 \text{ V} \checkmark$$

This is higher than the supply pd so this power dissipation so will not be reached  $\checkmark$

**OR**

Power dissipated when output is 5 V =  $4^2/250 = 0.064 \text{ W}$   $\checkmark$

Which is below the max power dissipation of 0.36 W  $\checkmark$

*$9^2/250 = 0.32 \text{ W}$  with incorrect conclusion scores 1*

*Second mark implies the first*

*$9^2/0.36 = 225 \Omega$  alone is not a useful calculation in the context. Still need to explain the effect of using the 250  $\Omega$*

*First mark is for a valid useful calculation*

(c) Use of potential divider formula to determine resistance of parallel combination  $\checkmark$

$$0.313 \text{ k}\Omega \checkmark$$

Use of equation for resistors in parallel  $\checkmark$

$$540 \Omega \checkmark$$

*Alternative to find resistance of combination*

*Current in circuit at room temp =  $4/250 = 16 \text{ mA}$   $\checkmark$*

*Resistance of combination =  $5/16\text{mA} = 313 \Omega$   $\checkmark$*

*OR*

$$\frac{V_{\text{combination}}}{V_{250}} = \frac{R_{\text{combination}}}{250}$$

$$\frac{5}{4} = \frac{R_{\text{combination}}}{250}$$

$$R_{\text{combination}} = 313 \Omega$$

**OR**

Current in circuit at room temp =  $4/250 = 16 \text{ mA}$   $\checkmark$

Current in thermistor =  $5/750 = 6.7 \text{ mA}$   $\checkmark$

Current in R =  $9.3 \text{ mA}$   $\checkmark$

$$R = 5/9.3 = 540 \Omega \checkmark$$

2sf answer  $\checkmark$

(only allowed with some relevant working leading to a resistor value)

Max 5

(d) Resistance of thermistor decreases ✓

Output pd decreases since

resistance of the parallel combination /circuit decreases

1

**OR**

lower proportion of pd across the parallel combination (or higher proportion across 250Ω)

**OR**

higher current so greater pd across the 0.25 k resistor ✓

*Accept correct consequences for R increasing with temperature for  
1 mark*

1

**[12]**

**6.**

(a) A combination of resistors in series connected across a voltage source  
(to produce a required pd) ✓

*Reference to splitting (not dividing) pd*

1

(b) When R increases, pd across R increases ✓

Pd across R + pd across T = supply pd ✓

So pd across T / voltmeter reading decreases ✓

*Alternative:*

Use of  $V = \frac{R_1 \times V_{tot}}{R_1 + R_2}$  ✓

*$V_{tot}$  and  $R_2$  remain constant ✓*

*So V increases when  $R_1$  increases ✓*

3

(c) At higher temp, resistance of T is lower ✓

1

So circuit resistance is lower, so current / ammeter reading increases ✓

1



(d) Resistance of T = 2500  $\Omega$

Current through T =  $V / R = 3 / 2500 = 1.2 \times 10^{-3} \text{ A}$  ✓

*(Allow alternative using  $V_1/R_1 = V_2/R_2$ )*

pd across R = 12 – 3 = 9 V

*The first mark is working out the current*

1

Resistance of R =  $V / I = 9 / 1.2 \times 10^{-3} = 7500 \Omega$  ✓

*The second mark is for the final answer*

1

(e) Connect the alarm across R instead of across T ✓

*allow: use a thermistor with a ptc instead of ntc.*

1

**[9]**