

M1.(a) A combination of resistors in series connected across a voltage source (to produce a required pd) ✓

Reference to splitting (not dividing) pd

1

(b) When R increases, pd across R increases ✓

Pd across R + pd across T = supply pd ✓

So pd across T / voltmeter reading decreases ✓

Alternative:

$$\frac{R_1 \times V_{tot}}{R_1 + R_2}$$

Use of $V = \frac{R_1 \times V_{tot}}{R_1 + R_2}$ ✓

V_{tot} and R_2 remain constant ✓

So V increases when R_1 increases ✓

3

(c) At higher temp, resistance of T is lower ✓

1

So circuit resistance is lower, so current / ammeter reading increases ✓

1

(d) Resistance of T = 2500 Ω

Current through T = $V / R = 3 / 2500 = 1.2 \times 10^{-3}$ A ✓

(Allow alternative using $V_1/R_1 = V_2/R_2$)

pd across R = 12 - 3 = 9 V

The first mark is working out the current

1

Resistance of R = $V / I = 9 / 1.2 \times 10^{-3} = 7500 \Omega$ ✓

The second mark is for the final answer

1

- (e) Connect the alarm across R instead of across T ✓
allow: use a thermistor with a ptc instead of ntc.

1
[9]

M2.B

[1]

- M3.(a) (i) (use of $I = V / R$)

first mark for adding resistance values 90 k Ω

$$I = 6.0 / (50\,000 + 35\,000 + 5000) \quad \checkmark = 6.7 \times 10^{-5} \text{ A} \quad \checkmark$$

accept 7×10^{-5} or dotted 6×10^{-5}

but not 7.0×10^{-5} and not 6.6×10^{-5}

2

- (ii) $V = 6.7 \times 10^{-5} \times 5000 \quad \checkmark = 0.33 \text{ (} 0.33 - 0.35 \text{) V} \quad \checkmark$
OR

$$V = 5 / 90 \times 6 \quad \checkmark = 0.33 \text{ (V)} \quad \checkmark$$

CE from (i)

BALD answer full credit

0.3 OK and dotted 0.3

2

- (b) resistance of LDR decreases ✓
need first mark before can qualify for second

reading increase because greater proportion / share of the voltage across R OR
higher current ✓

2

- (c) $I = 0.75 / 5000 = 1.5 \times 10^{-4} \text{ (A)} \quad \checkmark$
(pd across LDR = 0.75 (V))
pd across variable resistor = $6.0 - 0.75 - 0.75 = 4.5 \text{ (V)} \quad \checkmark$
 $R = 4.5 / 1.5 \times 10^{-4} = 30\,000 \Omega \quad \checkmark$
or
 $I = 0.75 / 5000 = 1.5 \times 10^{-4} \text{ (A)} \quad \checkmark$

$$R_{\text{total}} I = 6.0 / 1.5 \times 10^{-4} = 40\,000 \, \Omega \quad \checkmark$$

$$R = 40\,000 - 5000 - 5000 = 30\,000 \, \Omega \quad \checkmark$$

3
[9]

M4.(a) (i) $1/R_{\text{total}} = 1/(40) \checkmark + 1/(10+5) \checkmark = 0.09167$
 $R_{\text{total}} = 10.9 \, \text{k}\Omega \checkmark$

3

(ii) $I = 12 / 10.9 \, \text{k} = 1.1 \, \text{mA} \checkmark$

1

(b)

position	pd / V
AC	6.0 \checkmark
DF	4.0 \checkmark
CD	2.0 \checkmark

C.E. for CD

3

(c) (i) AC: no change \checkmark
 constant pd across resistors / parallel branches(AE) \checkmark
no CE from first mark

2

(ii) DF: decreases \checkmark
 as greater proportion of voltage across fixed / 10 k Ω resistor \checkmark
no CE from first mark

2

[11]

M5.(a) 1 joule per coulomb (or equivalent)

B1

allow watt per amp

1

(b) (i) Use of potential divider formula

C1

allow 1 for 4.05 (V) or current of 2.25 (mA)

4.95 (V)

A1

2

(ii) reduced current

B1

1

(iii) use of parallel resistor formula

C1

leading to 1.72 (k Ω)

C1

pd = 4.4 (V)

A1

3

(iv) potential divider can provides sensitive control of current (from 0 - 1.1 mA)

B1

*allow pot div can provide zero current **and** variable resistor gives larger current*

variable resistor can provide larger current but cannot get near 0 A owtte

B1

2

[9]

M6. (a) (i) (use of $V = IR$)

$$I = (12-8) / 60 \checkmark = 0.067 \text{ Or } 0.066(\text{A}) \checkmark$$

2

(ii) (use of $V = IR$)

$$R = 8/0.067 = 120 (\Omega) \checkmark$$

1

(iii) (use of $Q = It$)

$$Q = 0.067 \times 120 = 8.0 \checkmark \text{ C } \checkmark$$

2

(b) reading will increase \checkmark

resistance (of thermistor) decreases (as temperature increases) \checkmark

current in circuit increase (so pd across R_1 increases) OR correct potential divider argument \checkmark

3

[8]