

Q1. The circuit shown in **Figure 1** uses an ideal op-amp as a voltage comparator. It is used in a frost warning device in which the LED lights when the temperature falls to 0°C. **Figure 2** shows the variation of resistance with temperature of the thermistor.

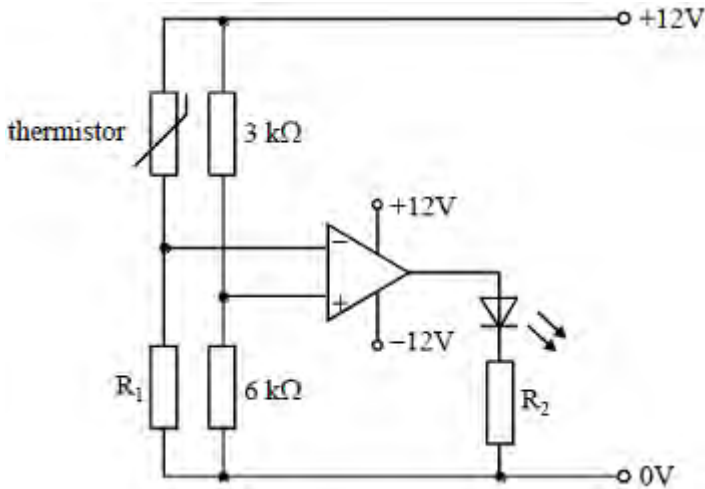


Figure 1

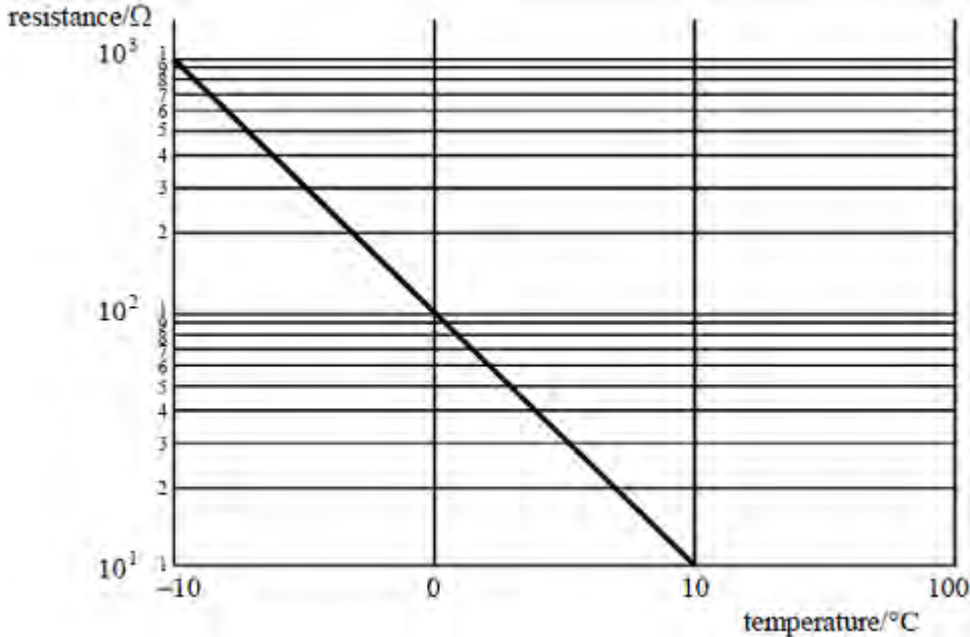


Figure 2

(a) Calculate the voltage at the non-inverting input of the op-amp.

.....
.....
.....
.....

(1)

(b) Calculate the resistance of R_1 to allow the output to switch at 0°C .

.....
.....
.....
.....

(2)

(c) When the LED is on, the current through it is 20 mA and the p.d. across it is 2.0 V.

Calculate

(i) the resistance of resistor R_2 ,

.....
.....

(ii) the power dissipated in this resistor.

.....
.....

(4)


(d) In practice, what value of resistor from the E24 series should be used for R_2 ?

.....

(1)

(Total 8 marks)

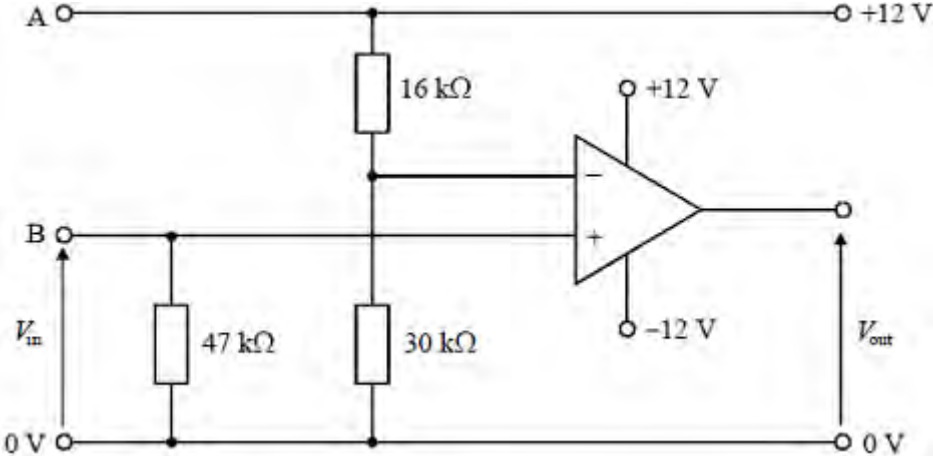Q2.In the circuit shown, an ideal operational amplifier is used as a voltage comparator.



(a) The voltage V_{in} is steadily increased from 0 V. Calculate V_{in} when the sign of V_{out} changes from negative to positive.

.....

.....

.....

(2)

(b) (i) The op-amp is required to operate an LED. Add to the circuit an LED and its limiting resistor so that the LED lights when V_{in} is less than the value calculated in part (a).

(ii) Explain why the LED functions in the position you have drawn it.

.....

.....


(iii) Calculate the minimum value for the limiting resistor with the LED. Assume that the LED has a voltage drop of 2.0 V across it when emitting and a maximum current of 25 mA through it.

.....

.....
.....

(5)

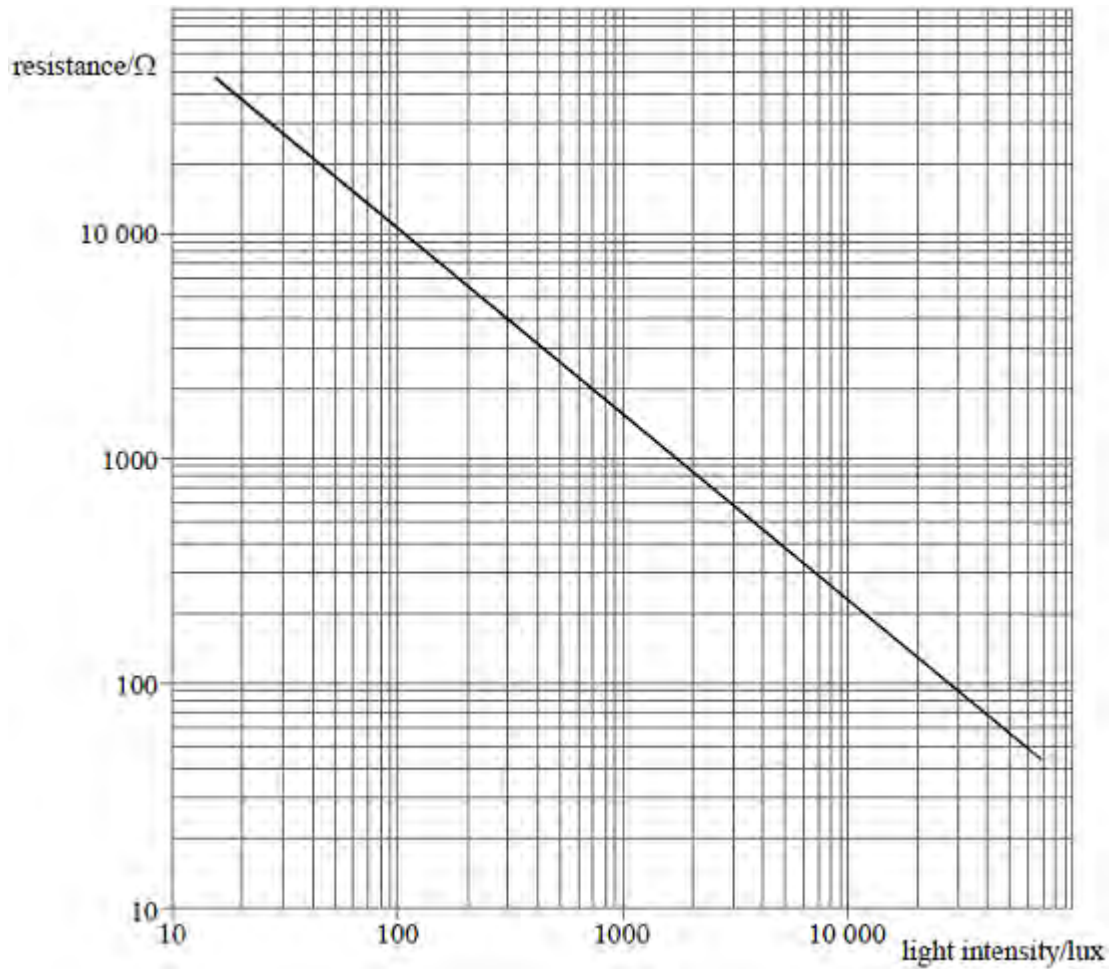- (c) An LDR is now connected between the points A and B in the circuit. The characteristic of the LDR is shown below.



Determine the light intensity at which the LED switches.

.....
.....
.....
.....
.....

(3)

Q3.(a) State **two** characteristics of an operational amplifier.

.....
.....

(2)

- (b) (i) Draw a circuit diagram showing an operational amplifier used as an inverting voltage amplifier.
- (ii) Give suitable values for the components you have used in the circuit for a voltage amplification of magnitude 150.

.....
.....
.....

(4)

(c) When *negative feedback* is used with an amplifier the bandwidth increases.

- (i) Explain what is meant by negative feedback as applied to the circuit drawn in part (b).

.....
.....
.....

- (ii) Give **one** other advantage of using negative feedback in this application.


.....

- (iii) State what is meant by the bandwidth of an amplifier.

.....
.....

(iv) Indicate on the graph below, by means of a horizontal line, the bandwidth of the amplifier whose characteristic is shown.

.....
.....

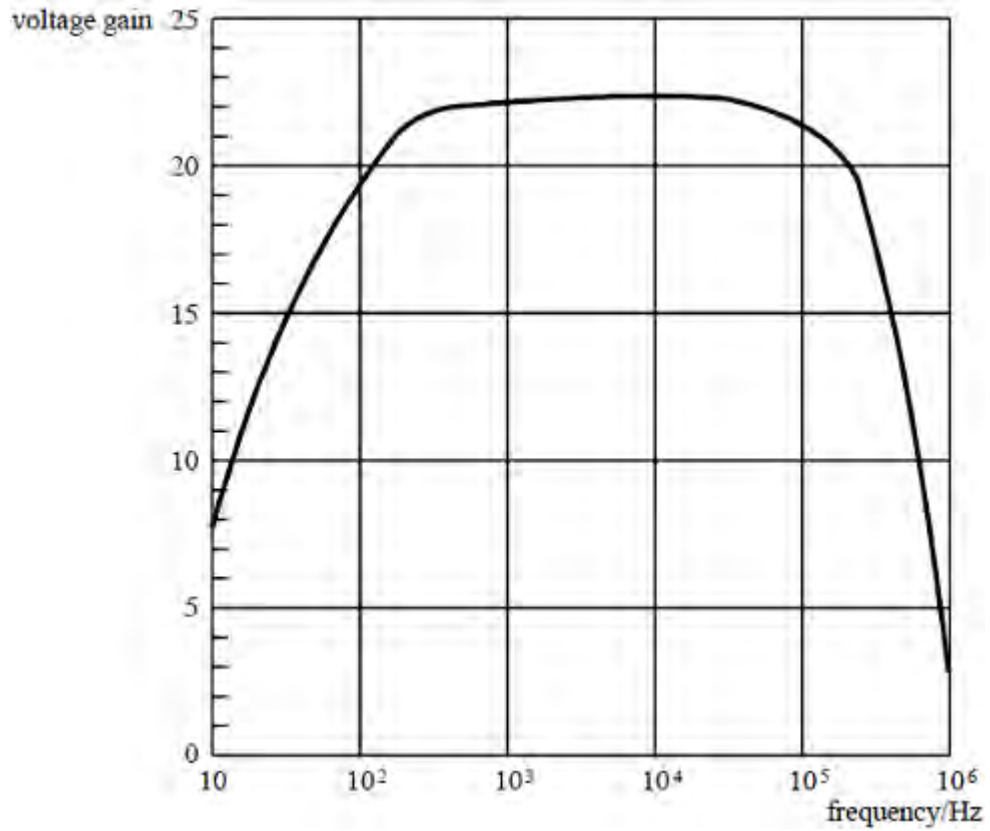

(5)
(Total 11 marks)